

# DLDCALab 1: Verilog

## Week 2

August 6, 2025

### Introduction

In this section you will be combining concepts from combinational and sequential programming.

### Necessary tools

We shall be using icarus-verilog alias iverilog inorder to compile verilog HDL. To visualise waveforms we shall use gtkwave.

Before starting the lab, ensure that both tools are installed in your system. This can be verified by running

```
$ iverilog
iverilog: no source files.
Usage: iverilog [-EiRSuvV] [-B base] [-c cmdfile|-f cmdfile]
             [-g1995|-g2001|-g2005|-g2005-sv|-g2009|-g2012] [-g<feature>]
             [-D macro[=defn]] [-I includedir] [-L moduledir]
             [-M [mode=]depfile] [-m module]
             [-N file] [-o filename] [-p flag=value]
             [-s topmodule] [-t target] [-T min|typ|max]
             [-W class] [-y dir] [-Y suf] [-l file] source_file(s)

See the man page for details.
$ gtkwave --version
GTKWave Analyzer v3.3.116 (w)1999-2023 BSI

GTKWAVE | Use the -h, --help command line flags to display help.
```

```
WM Destroy
```

## Structure of submission/templates

```
your-roll-no/  
|- outlab/  
    |- module.v (TODO)  
    |- testbench.v
```

The folder structure of the expected submission for this lab is given above. We expect this folder to be compressed into a tarball with the naming convention of your-roll-no.tar.gz. The command given below can be used to do the same

```
$ tar -cvzf your-roll-no.tar.gz your-roll-no/
```

In this task, you will build a modular Verilog design to cycle through a specific sequence of RGB colors. The final design will consist of a counter that cycles through 8 states, and a mapping from those states to specific 3-bit RGB output values.

The target RGB sequence is given in the table below:

| Cycle Number | Counter Value (3-bit) | RGB Output   |
|--------------|-----------------------|--------------|
| 0            | 000                   | 111 (White)  |
| 1            | 001                   | 010 (Blue)   |
| 2            | 010                   | 011 (Cyan)   |
| 3            | 011                   | 100 (Red)    |
| 4            | 100                   | 110 (Purple) |
| 5            | 101                   | 101 (Yellow) |
| 6            | 110                   | 001 (Green)  |
| 7            | 111                   | 000 (Black)  |

These are take home tasks that will help you finish the counter module. These are to be submitted by the end of this week.

### Task 1: Next-State Logic Module

Design a purely combinational module called getNextState that takes the current 3-bit counter value and produces the next value in binary sequence.

```
module getNextState (
```

```

        input  [2:0] currentState,
        output [2:0] nextState
    );

```

This module implements the next state logic for a 3-bit synchronous counter. Use toggle logic similar to T flip-flops, where each bit toggles based on the state of lower-order bits.

### Task 2: 3-bit Counter Module

Using the above next-state logic, implement a sequential module called `threeBitCounter` that updates the counter on each rising edge of the clock. Include a synchronous reset input that resets the counter to 000.

```

module threeBitCounter (
    input clk,
    input reset,
    output reg [2:0] count
);

```

You must use the `getNextState` module to compute the next value of the counter, and assign it synchronously on the rising edge of the clock.

### Task 3: Mapping Counter to RGB Lights

Design a combinational module called `counterToLights` that maps the binary counter value to a corresponding 3-bit RGB value according to the table above. Use only logic expressions. No arithmetic or control flow is allowed.

```

module counterToLights (
    input  [2:0] count,
    output [2:0] rgb
);

```

Use sum-of-products or direct logic expressions to define each RGB bit as a function of the 3-bit counter value.

For example on input count '000' the module should output rgb must be '111' according to the table.

#### **Task 4: Top-Level Module**

Create a top-level module called `rgbLighter` that connects all components. It should instantiate the counter and the color mapping module, and provide the final 3-bit RGB output.

```
module rgbLighter (  
    input clk,  
    input reset,  
    output [2:0] rgb  
);
```

You are expected to fill in the template code for all of the tasks and submit the same in the given format.